

1.0 Introduction

It is commonly known in the power community that powering microprocessors is becoming more difficult. This brief is intended to provide a mathematical statement describing one aspect of this increasingly difficult problem.

$$\frac{L}{C} \propto V^4$$

2.0 Background

The power consumption in microprocessors is related to two factors.

The first of these is termed leakage and constitutes about one fourth of the overall current draw. Leakage is the result of steady-state current flowing through all active devices as sort of a bias current. Leakage is not directly related to clock speed, but leakage current is growing as a result of the thinner oxide layers and operations closer to threshold voltages that are common in high-speed microprocessors.

The second major factor is related to microprocessor clock speed. Energy is lost every time a microprocessor elemental device switches between logic levels. This lost energy is required to charge or discharge the parasitic capacitance associated with each cell and mathematically can be expressed as $1/2 CE^2$ where C is the parasitic capacitance and E is the applied voltage. Since this phenomenon occurs with each clock cycle, calculating total power loss requires multiplying the loss by the microprocessor clock frequency making the power loss equal to $1/2CE^2F$, where F is the clock frequency.

With the losses increasing as the square of the applied voltage, it is clear the most direct path to lowering the overall power dissipation includes reducing the applied voltage. This makes it possible to add additional functionality to the microprocessor, while not increasing the power dissipation. The physics necessary to reduce the applied voltage is beyond the scope of this brief, but the need to reduce applied voltages for microprocessors as the industry moves into the future is a near certainty.

As can be seen in the next section, reducing the applied voltage creates a fourth order problem for the circuits providing power to microprocessors. It is this fourth order problem that has prompted industry leaders to identify power as the leading problem affecting efforts to advance the microprocessor functionality.

3.0 Derivation

For this derivation there are four assumptions:

1) The case under consideration is the worst case scenario – that being a downward step in current. In fact the limit case will be used for simplicity where the uP current is reduced from some fixed current to zero. In this case all the energy is transferred from the output inductance to the output capacitance.

2) The circuit contains only a VRM source with an output inductance L supplying a uP with a bypass capacitor C. With a MLCC bypass the series resistance and inductance of the bypass can be assumed to be so small they do not affect this analysis.

3) The power dissipation is constant. (Note: In reality the situation is actually may be more severe because the power dissipated in the heat sink may actually increase over time.)

4) The voltage tolerance expressed as a percent of the supply voltage is small (a few percent) and held constant. That is, $\Delta V/V = \text{constant}$.

$E1 = \text{Energy stored in output inductor} = \frac{1}{2} LI^2$.

$E2 = \text{Energy stored in output capacitor} = \frac{1}{2} CV^2$.

The starting point occurs when the energy in the inductor is transferred to the capacitor. The analysis is made when the current drawn from the uP goes to zero. This is a linear system easily analyzed at a limit condition. Small current changes will behave according to the same ratios.

$$E1 + E2 = \frac{C(V + \Delta V)^2}{2}$$

$$\frac{1}{2} LI^2 + \frac{1}{2} CV^2 = \frac{1}{2} C(V + V2)^2$$

$$LI^2 + CV^2 = C(V + V2)^2$$

$$= CV^2 + 2CV\Delta V + C\Delta V^2$$

Since $C\Delta V^2$ is a very small percentage, it is reduced to an insignificant number and can be removed.

3.0 Background Continued

$$= CV^2 + 2CV\Delta V$$

$$LI^2 = 2CV\Delta V$$

$$L = \frac{2CV\Delta V}{I^2}$$

$$\frac{L}{C} = \frac{2V\Delta V}{I^2}$$

Since power dissipation is a constant ($V \cdot I = \text{constant}$) and removing all other constants:

$$\frac{L}{C} \propto V^3 \Delta V$$

Since $\Delta V/V = \text{constant}$:

$$\frac{L}{C} \propto V^4$$

This is the, "Equation of pain".

4.0 Observations

The impedance of a VRM output filter must drop radically as the applied voltage to the microprocessor is reduced. This affects many current aspects of power design. One such area is the range of output voltage a VRM should be expected to accommodate. It is common for a VID (voltage identification data) table to cover a two-to-one range for output voltage. This is unnecessary, since there is no way for a VRM to accommodate the concomitant change in output impedance. Most VRM vendors already seem to know that this is not an appropriate voltage range, and some already optimize the VRM near the expected operating point.

The Ongoing Difficulty of Powering Microprocessors



Written by Bob Porter, VP of Engineering

About IKOR

IKOR, an iWatt Company, is a technology-driven supplier of power delivery solutions for original equipment manufacturers (OEMs) in the high-end computing, data communications and automated test equipment markets. IKOR products are designed and manufactured to exceed the rigorous performance, quality, and reliability requirements of our globally-recognized, top-tier customers.

Patent and Trademark Information

©2006 iWatt, Inc. All rights reserved. iWatt, the iW light bulb, IKOR, and POWER BRICK are registered trademarks of iWatt, Inc. All other trademarks and registered trademarks are the property of their respective owners.

The products and technology described in this data sheet include intellectual property covered by one or more of the following U.S. patents: 6,545,450; 6,686,727; 6,696,823. Purchase of this product from IKOR includes a royalty-free license to use and sell the intellectual property in the customer's end product on a per-unit basis. In no way does this license extend to customer end products which do not use this product to implement the intellectual property.

IKOR Contact Information

Web: <http://www.ikor-power.com>

E-mail: sales@ikor-power.com

Phone: 800-282-6100

Fax: 970-206-0716

IKOR, An iWatt Company

4424 Innovation Drive
Fort Collins, CO 80525 USA

Disclaimer

IKOR reserves the right to make changes to its products and to discontinue products without notice. IKOR makes no warranties other than those listed in its standard terms and conditions of sale and disclaims any implied warranties of non-infringement of third-party intellectual property rights.

IKOR is the owner and developer of power supply technology, including but not limited to coupled inductor technology and designs as described in US patents 6,545,450 6,686,727 and 6,696,823. The IKOR Coupled Inductor Design Guide provides a reference to implement designs into a VRD solution, using these patented technologies.

Upon request, IKOR may grant non-exclusive, non-transferable license to implement IKOR Product technology in VRD Designs, or make commercially reasonable efforts to assist in the promotion of the Products to mutually agreed prospective Customers. All demonstration and promotion of IKOR Product is restricted to approved IKOR designs, and shall be conducted using the IKOR brand name.

Certain applications may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

IKOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of IKOR products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to IKOR.